

$$(abcfa) + I_1 R_1 + V_1 - I_5 R_2 = 0$$

$$(cdetc) + V_2 - I_1 R_1 = 0$$

$$(yhcbg) + I_4 R_3 - V_3 = 0$$

$$\textcircled{c}: I_1 - I_2 - I_3 - I_4 = 0$$

$$\textcircled{b}: I_3 + I_4 + I_5 = 0$$



$$P = I_1^2 R_1 + I_2^2 R_2 + I_3^2 R_3$$

$$P = I^2 R = \frac{V^2}{R} = IV$$

$$I_1 = 20, \quad I_3 = -\frac{125}{6}, \quad I_5 = 12.5$$



$$P = (-I)^2 R = I^2 R$$

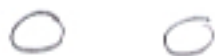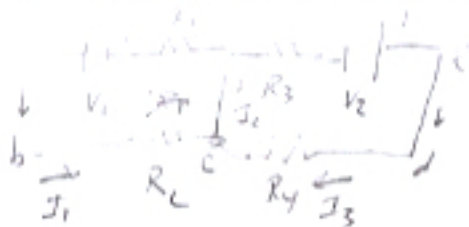




$$(abcfa): -I_1 R_2 - I_2 R_1 + V_1 = 0$$

$$(edcfe): -I_3 R_4 - I_3 R_3 + V_2 = 0$$

$$\textcircled{c}: I_1 + I_3 - I_2 = 0$$
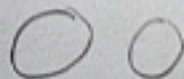
$$I_1 = \frac{V_1}{R_1 + R_2} \quad I_3 = \frac{V_2}{R_3 + R_4} \quad I_2$$



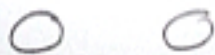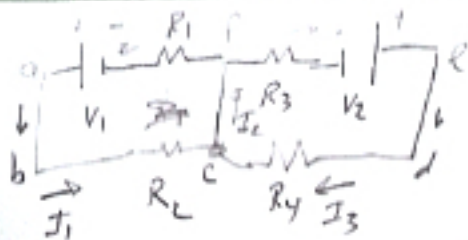

$$(abcfa): -I_1 R_2 - I_1 R_1 + V_1 = 0$$

$$(edcfe): -I_3 R_4 - I_3 R_3 + V_2 = 0$$

$$\text{at } c: I_1 + I_3 - I_2 = 0$$

$$I_1 = \frac{V_1}{R_1 + R_2} \quad I_3 = \frac{V_2}{R_3 + R_4}$$

