

(250)


$$U = \phi V \quad \phi \rightarrow \Delta V$$


$$P = \frac{dW}{dt} = V = \frac{d\phi}{dt} = IV \quad P = V \frac{d\phi}{dt}$$

$$V = IR \Rightarrow I = \frac{V}{R}$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

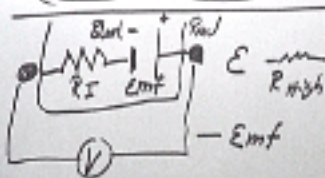

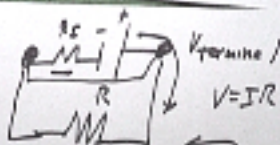

$$EMF - IR - I R_s = 0$$

$$V_{terminal} = E - I R_s$$

$$EMF = I(R + R_s)$$

$$I = \frac{EMF}{R + R_s}$$



$$C = \frac{1}{V} \Phi$$

$$\oint V_C + V_R = 0$$

$$V_C = \frac{\Phi}{C} \quad V_R = IR$$

$$\frac{\Phi}{C} + IR = 0 \Rightarrow \Phi + I(RC) = 0$$

$$R [\Omega] \frac{V}{A} \quad RC = \frac{C}{A} = \frac{C}{C/S} = S$$

$$L \quad \frac{S}{V}$$

$$V_C + V_R = 0$$

$$Q + I(RC) = 0$$

$$I = \frac{dQ}{dt}$$

$$Q + \frac{dQ}{dt}(RC) = 0$$

$$Q = -(RC) \frac{dQ}{dt}$$

$$\int \frac{-dt}{RC} = \int \frac{dQ}{Q}$$

$\frac{-t}{RC}$ $\ln\left(\frac{Q}{Q_0}\right)$

$$Q = -RC \frac{dQ}{dt}$$

$$\int_{\frac{t}{RC}}^{-\frac{dt}{RC}} = \int \frac{dQ}{Q}$$

$$-\ln\left(\frac{Q}{Q_0}\right)$$

$$\ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC}$$

$$\frac{Q}{Q_0} = e^{-t/RC} \quad RC = \tau$$

$$Q = Q_0 e^{-t/RC}$$

$$I = \frac{dQ}{dt} = -\frac{Q_0}{RC} \cdot e^{-t/RC}$$

$$C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C} = \frac{Q_0}{C} e^{-t/RC}$$

$$V_C + V_R = 0$$

$$Q + I(RC) = 0$$

$$I = \frac{dQ}{dt}$$

$$Q + \frac{dQ}{dt}(RC) = 0$$

$$Q = -(RC) \frac{dQ}{dt}$$

$$\int \frac{-dt}{RC} = \int \frac{dQ}{Q}$$

$\frac{t}{RC}$ $q \ln\left(\frac{Q}{Q_0}\right)$

$$\ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC}$$

$$\frac{Q}{Q_0} = e^{-t/RC} \quad RC = \tau$$

$$Q = Q_0 e^{-t/RC}$$

$$I = \frac{dQ}{dt} = -\frac{Q_0}{RC} \cdot e^{-t/RC}$$

$$C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C} = \frac{Q_0}{C} e^{-t/RC}$$

$$\vec{J} \quad \frac{\text{C}}{\text{m}^2 \cdot \text{s}}$$



$$\vec{J} = \frac{I}{A} \hat{x}$$



$$I = \oint \vec{J} \cdot d\vec{A}$$

$$V = IR$$

$$\vec{J} = \sigma \vec{E}$$


Conductivity

$$U = \frac{1}{2} CV^2$$



$$P = I^2 R$$

$$\vec{J} \quad \frac{C}{m^2}$$

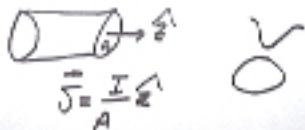

$$\vec{J} = \frac{I}{A} \hat{e}$$

$$I = \oint \vec{J} \cdot d\vec{A}$$

$$V = IR$$

$$\vec{J} = \sigma \vec{E}$$

conduction

$$U = \frac{1}{2} CV^2$$

$$\leftarrow \underline{m}$$

$$P = I^2 R$$



$$U_R = \int_{t=0}^{\infty} I^2 R dt \quad \left(P = \frac{dU}{dt} \right)$$

$$= \int_0^{\infty} \left(\frac{V_0}{R} e^{-t/RC} \right)^2 R dt$$

$$U_R = \int_{t=0}^{\infty} i^2 R dt \quad \left(p = \frac{dU}{dt} \right)$$

$$= \int_0^{\infty} \left(\frac{V_0}{R} e^{-t/RC} \right)^2 R dt$$
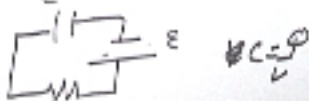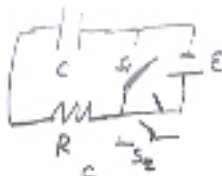
$$\therefore \int_0^{\infty} e^{-2t/RC} dt \rightarrow \frac{1}{2} CV^2$$



$$R \quad \mathcal{E} - IR - \frac{dQ}{dt} = 0$$

$$V = \mathcal{E} - \frac{Q}{C} e^{-t/RC}$$

$$C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C}$$

$$Q = C \left[\mathcal{E} - \frac{Q}{C} e^{-t/RC} \right]$$

$$I = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$


$$(1) \begin{array}{c} R_1 \quad R_2 \\ \text{---} \text{---} \text{---} \rightarrow 0.1A \\ 10\Omega \quad 100\Omega \end{array}$$

$$P = I^2 R$$

$$P_{R_1} = (.1)^2 \times 10 = .1 W$$

$$P_{R_2} = (.1)^2 \times 100 = 1 W$$

$$P = P_1 + P_2 = 1.1 W$$

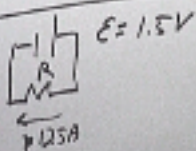


$$E - IR_I - IR = 0$$

$$E - IR = IR_I$$

$$R_I = \frac{E - IR}{I} = \frac{1.5 - .125(10)}{.125}$$

$$P_{R_2} = (-1)^2 \times 100 = 1 \text{ W}$$

$$P = P_1 + P_2 = 1.1 \text{ W}$$

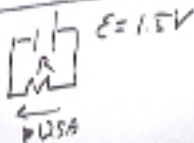

$$E - IR - IR = 0$$

$$E - IR = IR$$

$$R = \frac{E - IR}{I} = \frac{1.5 - 0.125(10)}{0.125}$$