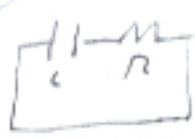


250



$$Q = Q_0 e^{-t/\tau}$$

$$\tau = RC$$

$$I = \frac{dQ}{dt} = -\frac{Q_0}{\tau} e^{-t/\tau}$$

$$C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C}$$



$$V = -\frac{Q_0}{\tau C} e^{-t/\tau}$$

$$V = \mathcal{E}(1 - e^{-t/\tau})$$

$$Q = CV$$

$$I = dQ/dt$$

R


~~K = I^2 R~~

$$U = QV$$

$$P = \frac{dU}{dt} = IV = I^2 R = \frac{V^2}{R}$$

$\Delta \delta \propto \delta$

2.2

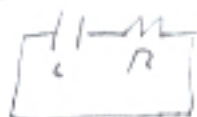


$$Q = Q_0 e^{-t/\tau}$$

$$\tau = RC$$

$$I = \frac{dQ}{dt} = -\frac{Q_0}{\tau} e^{-t/\tau}$$
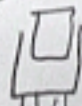
$$C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C}$$



$$V = -\frac{Q_0}{\tau C} e^{-t/\tau}$$

$$V = \mathcal{E}(1 - e^{-t/\tau})$$

$$Q = CV$$

$$I = dQ/dt$$

~~V = IR~~

$$U = QV$$

$$P = \frac{dU}{dt} = IV = I^2 R = \frac{V^2}{R}$$

$$\Delta \delta \propto \delta$$

$$\delta = \# \rho^{-ct}$$

$$I \rightarrow \frac{V}{R} \quad V = IR$$

$$U = QV$$

$$P = \frac{dU}{dt} = IV = I^2 R = \frac{V^2}{R}$$

$$\Delta t \propto \frac{1}{P}$$

$$\frac{1}{P} = \frac{1}{I^2 R}$$

$$Q = Q_0 e^{-t/\tau}$$


$$\frac{Q}{Q_0} = \frac{1}{2} = e^{-t_{1/2}/\tau}$$

$$-\ln(2) = -t_{1/2}/\tau$$

$$t_{1/2} = \tau \ln(2)$$

$$\sum V_i = 0$$

$$\sum I_i = 0$$

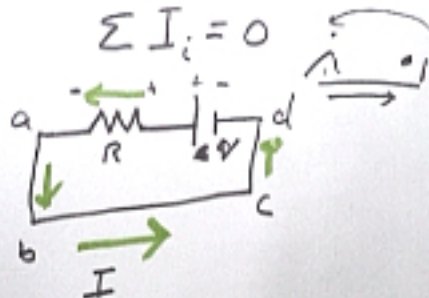

$\rightarrow + +V$ in dir: $-IR$


$\leftarrow - -V$ in opposite dir of I: $+IR$

$$+V - IR = 0 \quad V = IR$$

$$I = \frac{V}{R}$$

$$\sum V_i = 0$$

$$\sum I_i = 0$$

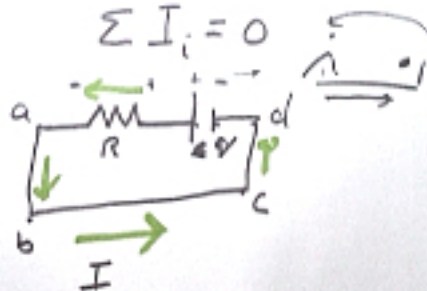


$\rightarrow + +V$ in dir: $-IR$

$\leftarrow - -V$ in opposite dir of I : $+IR$

$$+V - IR = 0 \quad V = IR$$

$$I = \frac{V}{R}$$
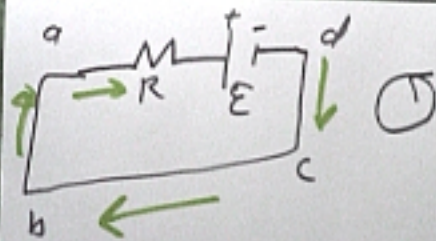
$$\begin{aligned}
 & \xrightarrow{-} + +V \quad \text{in dir: } -IR \\
 & \xrightarrow{+} - -V \quad \text{in opposite} \\
 & \quad \quad \quad \text{dir of } I : +IR \\
 & +V - IR = 0 \quad V = IR \\
 & \quad \quad \quad I = \frac{V}{R}
 \end{aligned}$$



$$\begin{aligned}
 (abcd) \quad \Sigma V &= 0 + 0 + \\
 & + \varepsilon + IR = 0
 \end{aligned}$$


$$\begin{aligned}
 \varepsilon + IR &= 0 \Rightarrow I = -\frac{\varepsilon}{R} \\
 \rightarrow
 \end{aligned}$$

$$\mathcal{E} + IR = 0 \Rightarrow I = -\frac{\mathcal{E}}{R}$$



$$(abcd) = +IR - V = 0$$

$$I = \frac{V}{R}$$

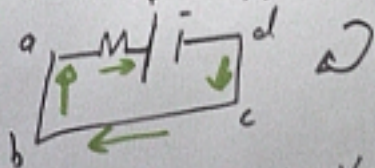


$$(adcb): -IR - V = 0$$

$$I = -\frac{V}{R}$$

$$\mathcal{E} + IR = 0 \Rightarrow I = -\frac{\mathcal{E}}{R}$$





$$(abcd) = +IR - V = 0$$

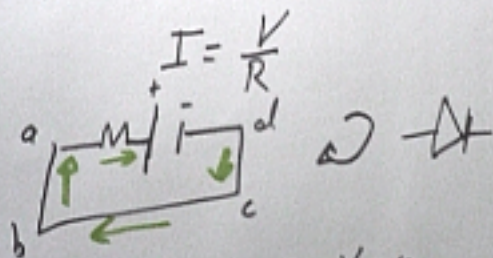

$$(adcb): -IR - V = 0$$

$$I = -\frac{V}{R}$$

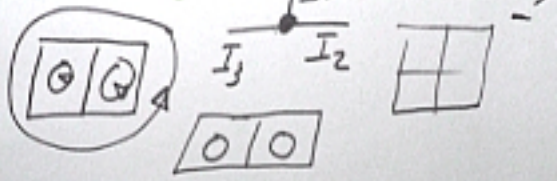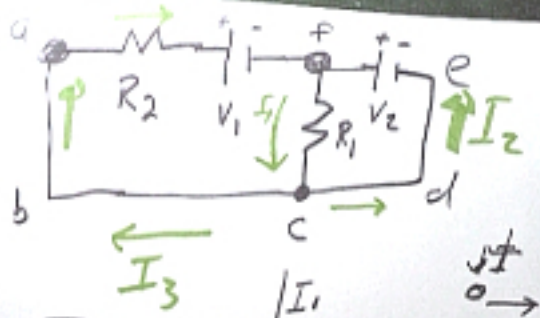

$(abcfa): +I_1 R_1 + V_1 - I_3 R_2 = 0$
 $(fcdef): -I_1 R_1 + V_2 = 0$
 $\odot C: +I_1 - I_2 - I_3 = 0$



$$(abcfa): +I_1 R_1 + V_1 - I_3 R_3 = 0$$

$$(fcdef): -I_1 R_1 + V_2 = 0$$

$$\textcircled{c} C: +I_1 - I_2 - I_3 = 0$$

$$-I_1 R_1 = -V_2 \Rightarrow I_1 = \frac{V_2}{R_1}$$

$$\frac{V_2}{R_1} R_1 + V_1 - I_3 R_3 = 0$$

$$V_2 + V_1 = I_3 R_3$$

$$I_3 = \frac{V_2 + V_1}{R_3}$$

$$I_2 = \frac{V_2}{R_1} - \frac{(V_2 + V_1)}{R_3}$$

$$P = I_1^2 R_1 + I_3^2 R_3$$