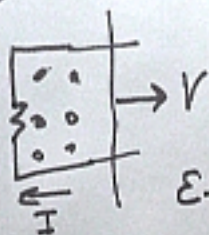


250



$$\mathcal{E} = -\frac{d\Phi_M}{dt}$$

$$\Phi_M = B \cdot W \cdot x \quad x = x_0 + ct^3$$

$$\frac{d\Phi_M}{dt} = BW \frac{dx}{dt} \Big| \frac{dx}{dt} = 3ct^2$$

$$|\mathcal{E}| = BW \cdot 3ct^2$$

$$I = \frac{|\mathcal{E}|}{R} = \frac{3BWct^2}{R}$$




$$v = V_m \sin(\omega t)$$


$$\omega = 2\pi f$$

$$i = \frac{V_r}{R} = \frac{V_m \sin(\omega t)}{R}$$

$$I_m = \frac{V_m}{R}$$

$$V_r = I_m R \sin(\omega t)$$

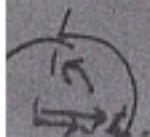

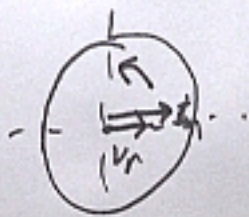


$$p = i^2 R$$

$$\langle p \rangle = \langle i^2 R \rangle = I_m^2 R \underbrace{\langle \sin^2(\omega t) \rangle}_{\frac{1}{2}}$$

$$\langle p \rangle = \frac{1}{2} I_m^2 R$$

$$V_{RMS} = \frac{V_m}{\sqrt{2}} \quad I_{RMS} = \frac{I_m}{\sqrt{2}}$$

$$\langle p \rangle = V_{RMS} I_{RMS}$$

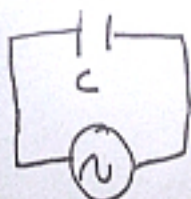


$$V = V_m \sin(\omega t)$$

$$C = \frac{Q}{V} \Rightarrow Q = CV$$

$$\frac{dQ}{dt} = C \frac{dV}{dt} = C \cdot \omega V_m \cos(\omega t)$$
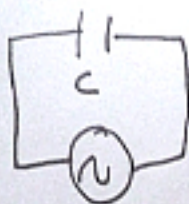
$$\Rightarrow i_c = \omega C V_m \sin\left(\omega t + \frac{\pi}{2}\right)$$




$$V = V_m \sin(\omega t)$$

$$C = \frac{Q}{V} \Rightarrow Q = CV$$

$$\frac{dQ}{dt} = C \frac{dV}{dt} = C \cdot \omega V_m \sin(\omega t)$$
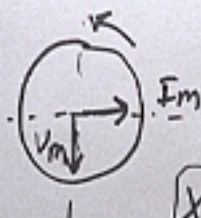
$$\Rightarrow i_c = \omega C V_m \sin(\omega t + \frac{\pi}{2})$$







$$I_m = \omega C V_m$$

$$X_C = \frac{1}{\omega C} \quad \begin{array}{l} \text{Capacitive} \\ \text{Reactance} \end{array}$$

$$V_m = I_m X_C$$
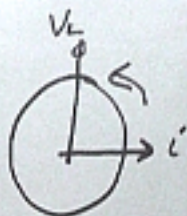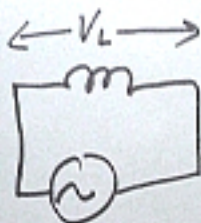
$$\Rightarrow V_C = I_m X_C \sin(\omega t)$$



$$V = V_m \sin(\omega t)$$


$$\mathcal{E} = -L \frac{di}{dt}$$

$$i_L = -\frac{V_m}{\omega L} \cos(\omega t)$$

$$\Rightarrow i_L = \frac{V_m}{\omega L} \sin\left(\omega t + \frac{\pi}{2}\right)$$

~~$$X_L = \omega L$$~~

$$\underline{X_L = \omega L}$$

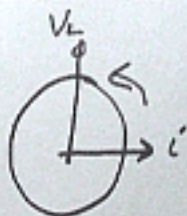

$$V = V_m \sin(\omega t)$$





$$\mathcal{E} = -L \frac{di}{dt}$$

$$i_L = -\frac{V_m}{\omega L} \cos(\omega t)$$

$$\Rightarrow i_L = \frac{V_m}{\omega L} \sin\left(\omega t + \frac{\pi}{2}\right)$$

~~$$X_L = \omega L$$~~

$$\underline{X_L = \omega L}$$

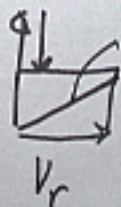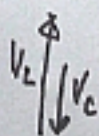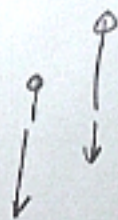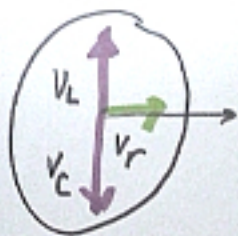

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V_R = I_m R \quad V_C = I_m X_C$$

$$V_L = I_m X_L$$

$$V_R = I_m R \quad V_C = I_m X_C$$

$$V_L = I_m X_L$$

$$V = \cancel{I_m \sqrt{R^2 + X_C^2}}$$

$$V = I_m \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V = I_m Z$$

$$\cos \phi = \frac{R}{Z}$$

$$P = IV \cos \phi$$

$$V_R = I_m R \quad V_C = I_m X_C$$

$$V_L = I_m X_L$$

$$V = I_m \sqrt{R^2 + (X_L - X_C)^2}$$

$$V = I_m \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V = I_m Z$$

$$\cos \phi = \frac{R}{Z}$$

$$P = IV \cos \phi$$

$$Z = \sqrt{R^2 + \underbrace{(X_L - X_C)^2}$$

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega_{res} = \frac{1}{\sqrt{LC}}$$

\underline{m}

$\perp \perp$

Lf: ---

Lf: $\text{---} \setminus$


$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

Hf: $\text{---} \setminus$

Hf: ---

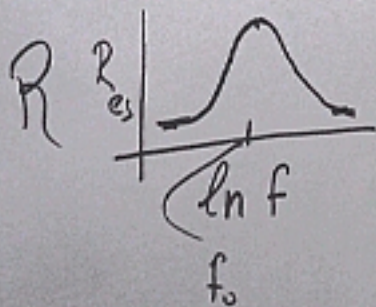$\overset{C}{m} / \overset{C}{H} \overset{R}{M}$



$\text{---} \setminus \perp$